
Table of Contents

This file implement the ELEC 4700 PA7	1
a) Create the C, G matrices	1
b) DC sweep input voltage from -10V to 10V and plot V0 and V3 (N3)	2
c) AC case plot Vo as a function of omega and plot the gain Vo/V1 in dB	3
d) Plot gain as a random perturbations on C at omega=pi	5

This file implement the ELEC 4700 PA7

Goal: Do a DC and AC analysis of a linear circuit using MNA techniques

```
% Clear all
clearvars
clearvars -global
close all

% Save some component values
R1 = 1;
C = 0.25;
R2 = 2;
L = 0.2;
R3 = 10;
alpha = 100;
R4 = 0.1;
RO=1000;

% Declare the vectors
vectorV = zeros(9, 1); % solution vector: [N1, N2, N3, N4, N5, I1, IL, I3,
    I4]
vectorF = zeros(9, 1); % F vector: F(1) = VIN
```

a) Create the C, G matrices

Declare the C matrix

```
matrixC = [0, 0, 0, 0, 0, 0, 0, 0, 0;
    C, -C, 0, 0, 0, 0, 0, 0, 0;
    -C, C, 0, 0, 0, 0, 0, 0, 0;
    0, 0, 0, 0, 0, 0, -L, 0, 0;
    0, 0, 0, 0, 0, 0, 0, 0, 0;
    0, 0, 0, 0, 0, 0, 0, 0, 0;
    0, 0, 0, 0, 0, 0, 0, 0, 0;
    0, 0, 0, 0, 0, 0, 0, 0, 0;
    0, 0, 0, 0, 0, 0, 0, 0, 0];

% Declare the G matrix
matrixG = [1, 0, 0, 0, 0, 0, 0, 0;
    1/R1, -1/R1, 0, 0, 0, 0, 0, 0;
    0, 0, 1, 0, 0, 0, 0, 0;
    0, 0, 0, 1, 0, 0, 0, 0;
    0, 0, 0, 0, 1, 0, 0, 0;
    0, 0, 0, 0, 0, 1, 0, 0;
    0, 0, 0, 0, 0, 0, 1, 0;
    0, 0, 0, 0, 0, 0, 0, 1];
```

```

-1/R1, 1/R1+1/R2, 0, 0, 0, 0, 1, 0, 0;
0, 1, -1, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, -1, 1, 0;
0, 0, -1/R3, 0, 0, 0, 0, 1, 0;
0, 0, 0, 1/R4, -1/R4, 0, 0, 0, 1;
0, 0, 0, 1, 0, 0, 0, -alpha, 0;
0, 0, 0, -1/R4, 1/R4+1/RO, 0, 0, 0, 0];


```

b) DC sweep input voltage from -10V to 10V and plot V0 and V3 (N3)

```

simStep = 21; % Simulation steps
V1 = linspace(-10, 10, simStep); % vector for input voltages
Vo = zeros(simStep, 1); % vector for holding the output voltage
V3 = zeros(simStep, 1); % vector for holding the voltage at V3
% Loop for the DC simulation
for iSim = 1:simStep
    % Setup the F vector
    vectorF(1) = V1(iSim); % Stepup the input voltage
    % Find the solution
    vectorV = matrixG\vectorF;
    % Save answers
    Vo(iSim) = vectorV(5); % Save Vout
    V3(iSim) = vectorV(3); % Save V3
end
% Plot the DC simulation
figure(1)
hold on
plot(V1, Vo, "-b.")
plot(V1, V3, "-r.")
title("DC simulation")
xlabel("Vin (V)")
ylabel("Vout and V3 (V)")
legend("Vout", "V3")
grid on;

```

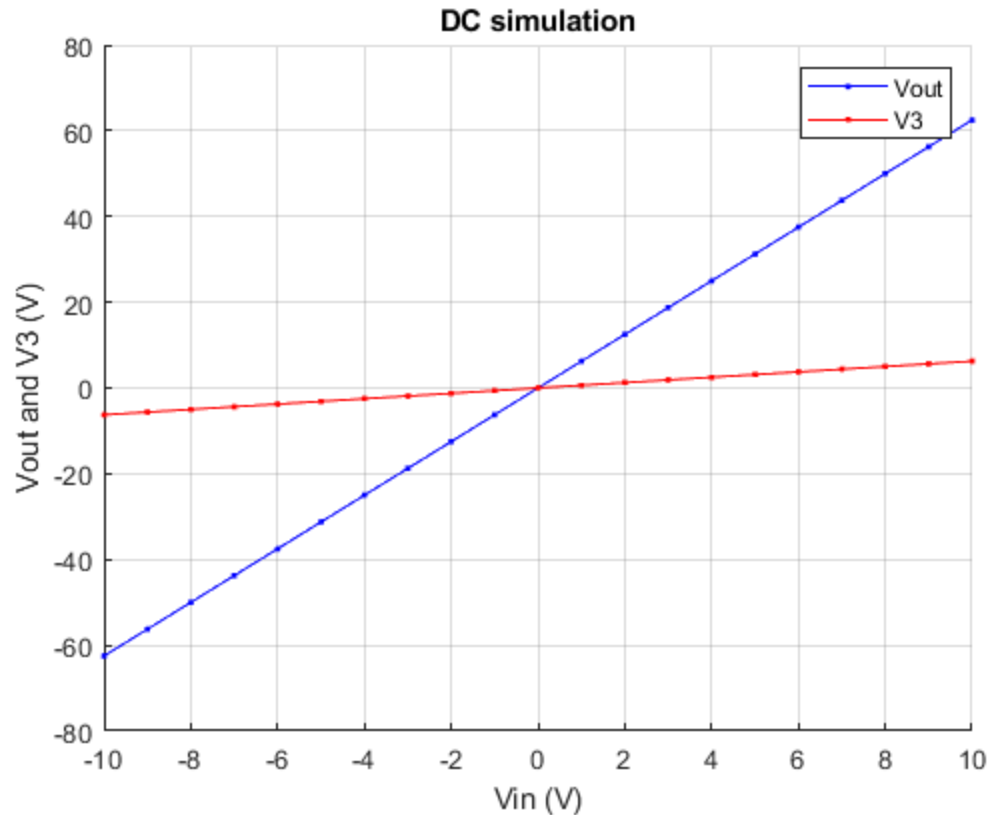

c) AC case plot V_o as a function of ω and plot the gain V_o/V_1 in dB

```
simSteps = 100; % Simulation steps
Vin = 1; % Value for input voltage
vectorF(1) = Vin; % Setup the input voltage
omega = linspace(1, 100, simSteps); % vector for frequencies
Vo = zeros(simSteps, 1); % vector store the output voltages
V3 = zeros(simStep, 1); % vector for holding the voltage at V3


% Loop for simulation
for iSim = 1:simSteps
    w = omega(iSim); % Retrieve the simulation frequency
    % Construct the G+jwC matrix
    matrixGC = matrixG + 1j*w*matrixC;
    % Find the solution
    vectorV = matrixGC\vectorF;
    % Save answers
    Vo(iSim) = abs(vectorV(5)); % Save Vout
    V3(iSim) = abs(vectorV(3)); % Save V3
end
% Plot Vo as a function of omega
figure(2)
hold on
```


```

plot(omega, Vo, "-b.");
plot(omega, V3, "-r.");
title("Vo as a function of omega")
xlabel("Frequency omega (rad/s)")
ylabel("Vout (V)")
legend("Vout", "V3")
grid on

% Plot the gain Vo/V1 in dB
figure(3)
gain = 20*log10(Vo ./ Vin); % Calculate the gain in dB
plot(omega, gain);
title("Gain Vo/V1 in dB versus omega")
xlabel("Frequency omega (rad/s)")
ylabel("Gain (dB)")
grid on

```

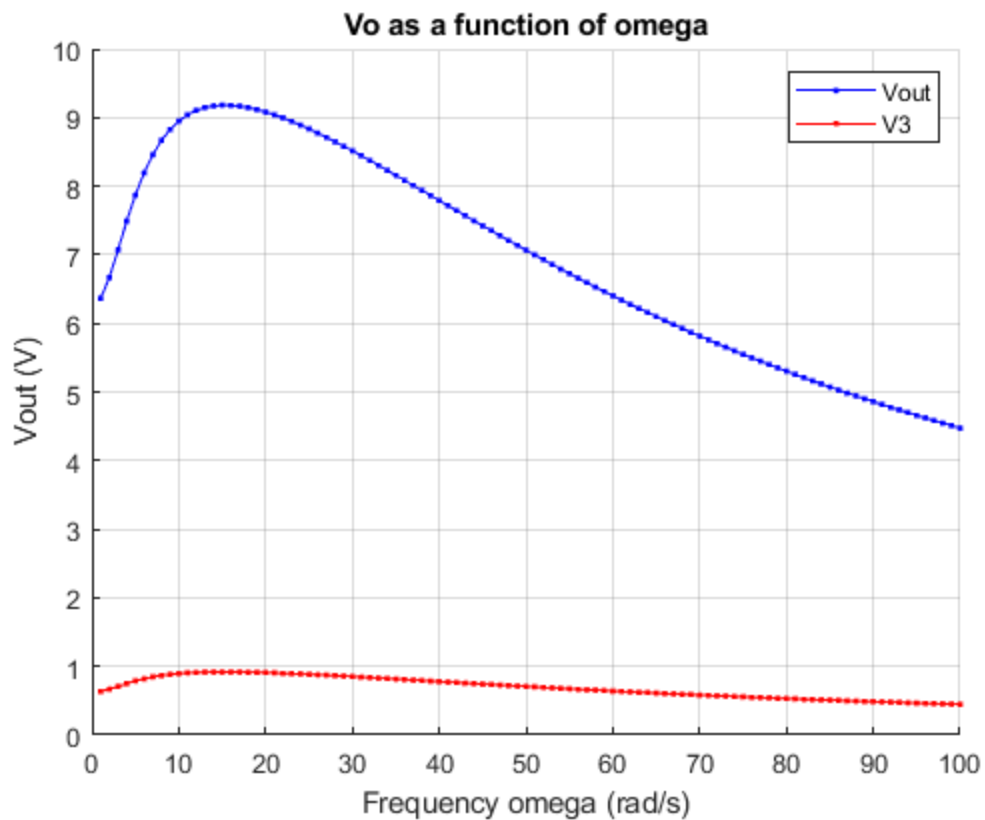

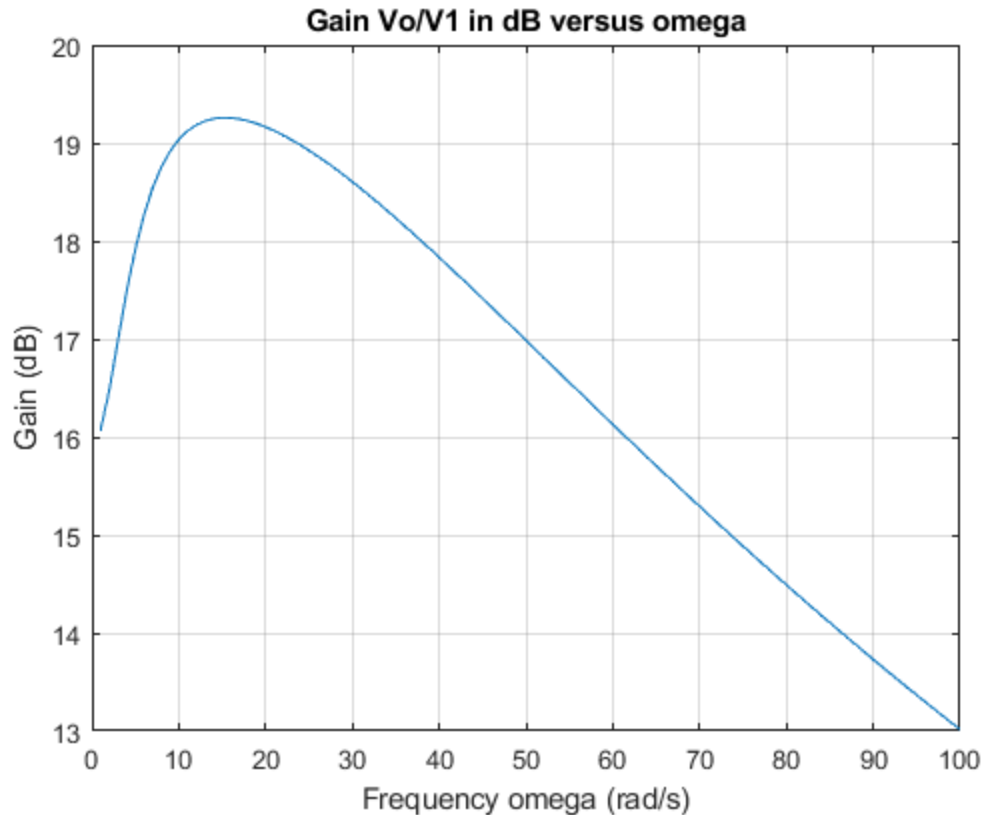

d) Plot gain as a random perturbations on C at $\omega = \pi$

```
simSteps = 1000; % Simulation steps
omega = pi;
std = 0.05; % Standard deviation of the normal distribution
randomC = std .* randn(simSteps, 1)+C; % vector store the random C
Vo = zeros(simSteps, 1); % vector store the output voltages
Vin = 10; % Value for input voltage
vectorF(1) = Vin; % Setup the input voltage

% Plot the normal distribution of C
nbins = 10; % Number of bins for the histogram
figure(5)
histogram(randomC, nbins);
title("Distribution of C")
xlabel("C")
ylabel("Number")
grid on

% Loop through the random C
for iSim=1:simSteps
    C = randomC(iSim); % Retrieve the C value
    % Reconstruct the C matrix
```


```


matrixC = [0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
C, -C, 0, 0, 0, 0, 0, 0, 0, 0;
-C, C, 0, 0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, -L, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, 0, 0];

% Construct the G+jwC matrix
matrixGC = matrixG + 1j*omega*matrixC;
% Find the solution
vectorV = matrixGC\vectorF;
% Save answers
Vo(iSim) = abs(vectorV(5)); % Save Vout
end

% Plot the distribution of gain
figure(6)
gain = Vo ./ Vin; % Calculate the gain
histogram(gain, nbins);
title("Distribution of Gain")
xlabel("Vo/Vi")
ylabel("Number")
grid on

```

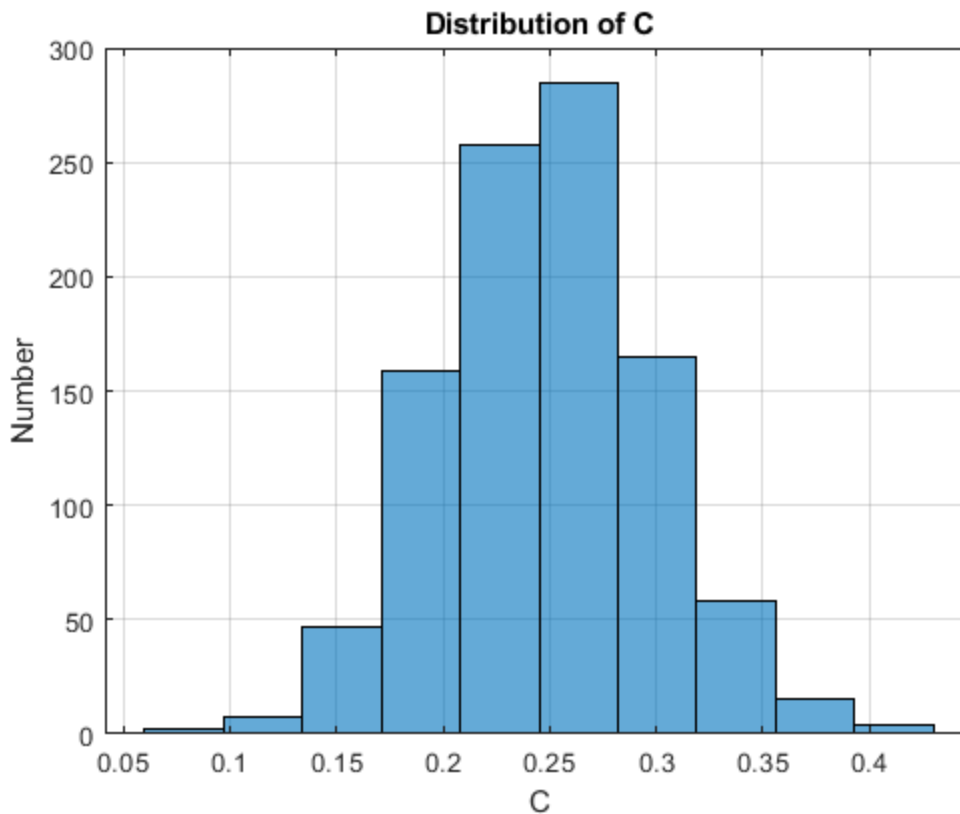

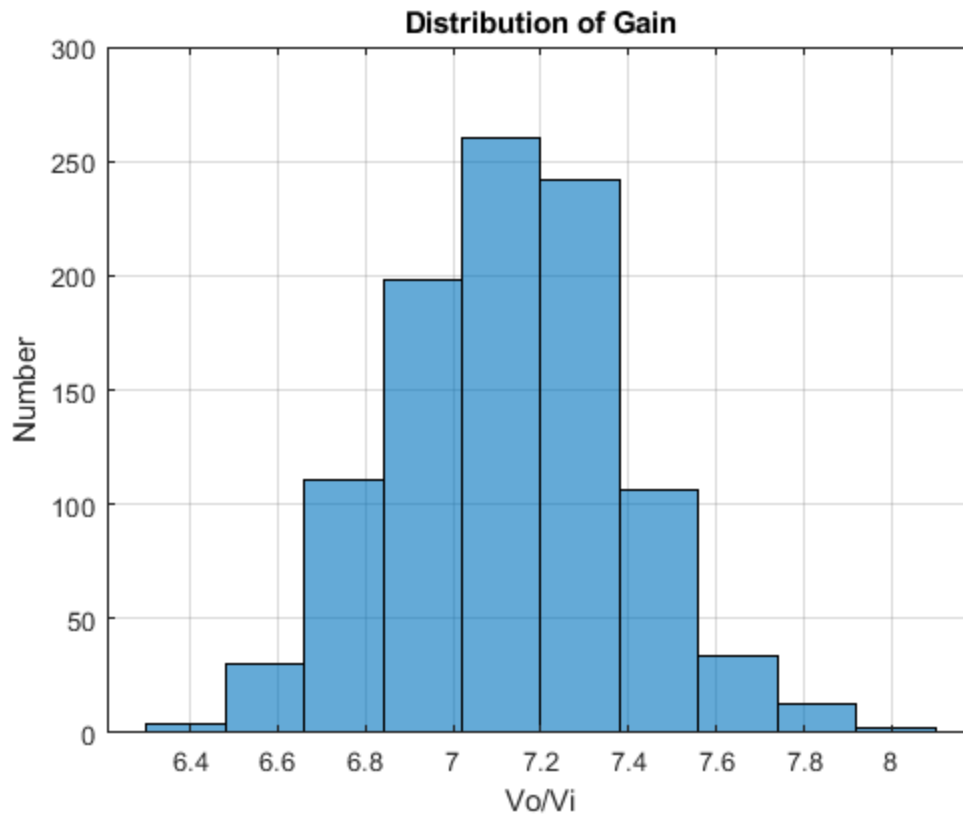

Published with MATLAB® R2021b